

ECE 3113 - Energy Conversion

Homework 1

(Due on Friday 09/08/2023)

1. With the appropriate trigonometric identities and some math derivations, find the value of:

$$\sin(\omega t) + \sin(\omega t - 2\pi/3) + \sin(\omega t + 2\pi/3)$$

Explain the engineering intuition behind this mathematic derivation.

2. Derive the instantaneous power for following instantaneous current and voltage.

$$v(t) = 140 \cos(120\pi t + 25^\circ)$$

$$i(t) = 14 \cos(120\pi t - 78^\circ)$$

3. Find the current I_L in the following scenarios:

- 1) $Z=500 \text{ Ohm}$ and is at location a)
- 2) $Z=j500 \text{ Ohm}$ and is at location b)
- 3) $Z=-j500 \text{ Ohm}$ and is at location c)

