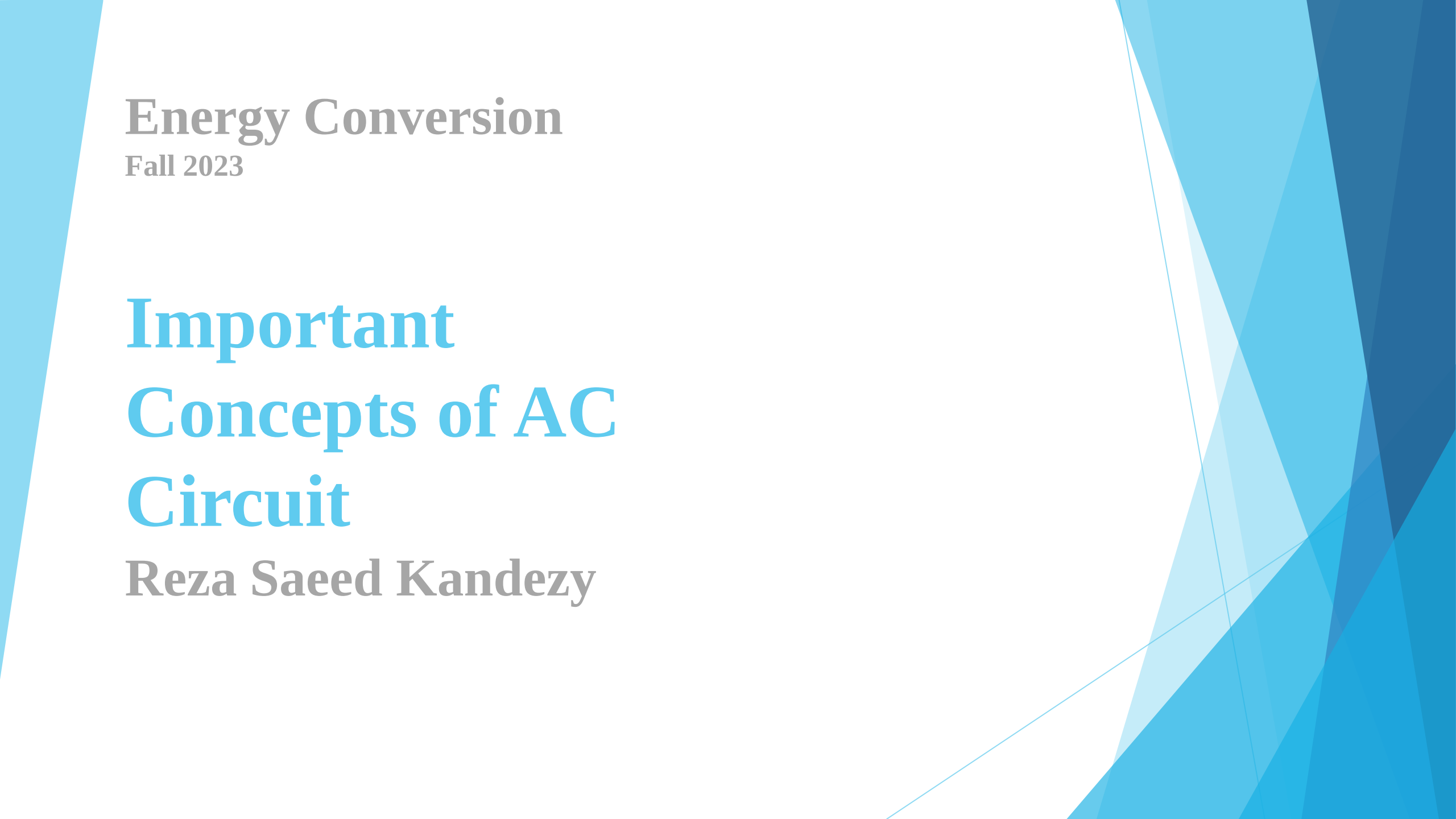


The background features abstract, overlapping geometric shapes in various shades of blue, ranging from light sky blue to deep navy blue. These shapes are primarily located on the left and right sides of the slide, framing the central white area where the text is placed.

Energy Conversion

Fall 2023


**Important
Concepts of AC
Circuit**

Reza Saeed Kandezy

Summary

- ▶ **Major variables in AC circuit: current (i), voltage (v), power (S, P, Q)**
 - Parameters of the variables (amplitude, frequency, & phase)
 - Representations of the major variables
 - Complex number
 - Trigonometric functions
 - Phasor
 - Phase displacement
 - Where the phase displacement comes from
 - Impact of phase displacement
 - Impedance triangle
 - Lagging, leading, in-phase current with respect to the voltage
- ▶ **Power**
 - Instantaneous Power
 - Average (Active) and Reactive Power
 - Complex Power and Power triangle
 - Power factor
- ▶ **Examples**

Important Concepts of AC Circuit

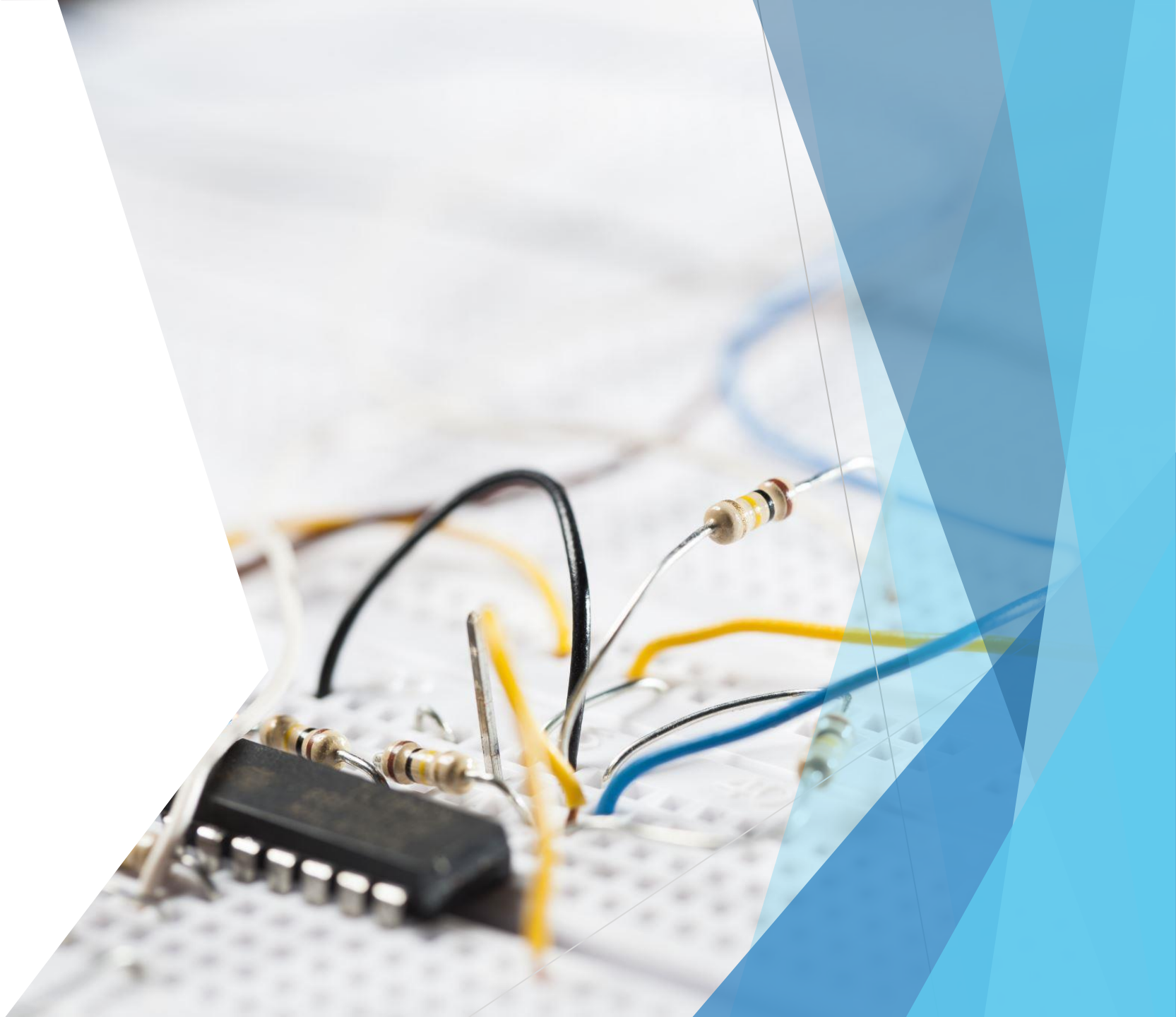

AC vs. DC Circuit

$V(t) = \text{constant},$




$I(t) = \text{constant}.$

→ DC Electric circuit → DC Magnetic circuit

$V(t) \neq \text{constant},$

$I(t) \neq \text{constant}.$

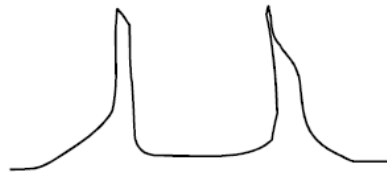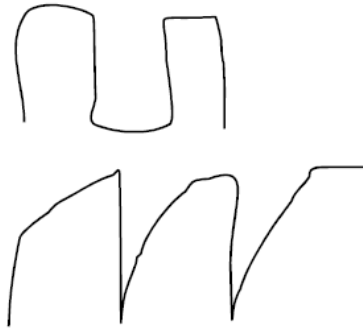
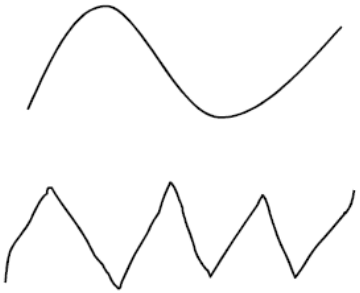
→ AC circuit → AC Magnetic circuit
if not saturated



AC vs. DC Circuit

$V(t) = \text{constant},$
 $I(t) = \text{constant.}$ $\longrightarrow$ DC Electric circuit $\longrightarrow$ DC Magnetic circuit

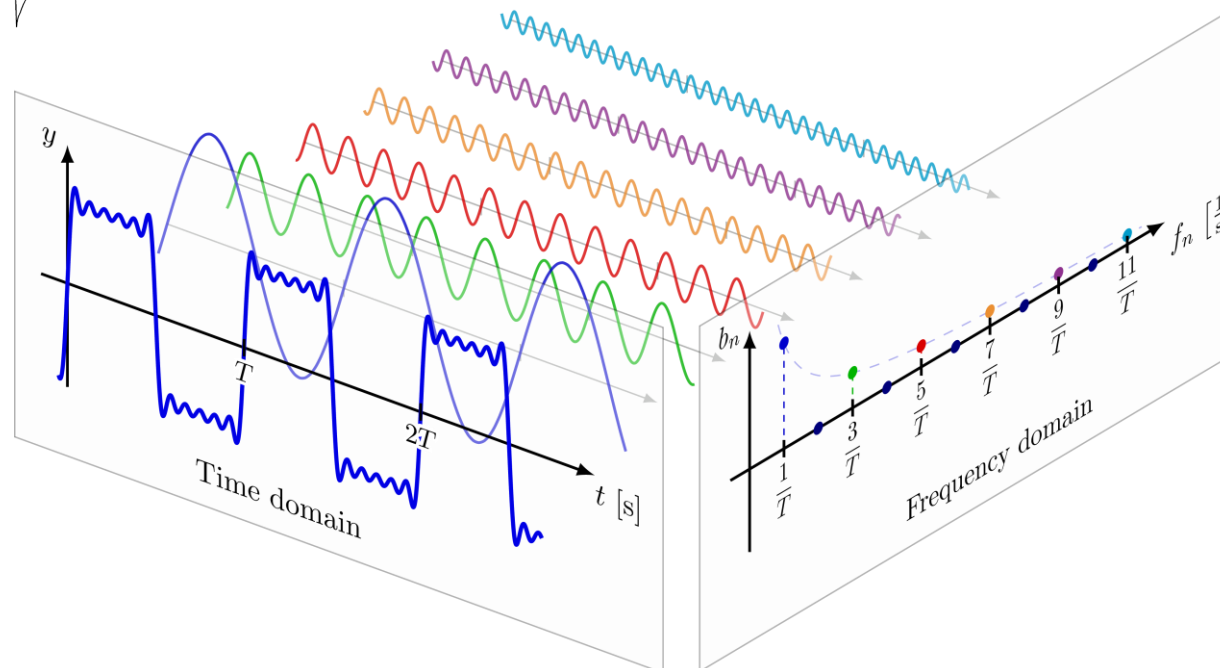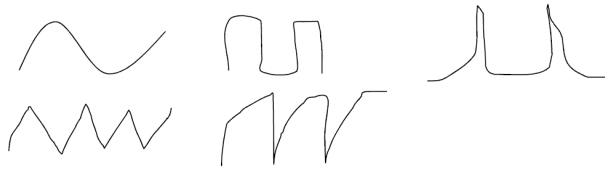$V(t) \neq \text{constant},$
 $I(t) \neq \text{constant.}$ $\longrightarrow$ AC circuit $\longrightarrow$ AC Magnetic circuit
if not saturated




http://upload.wikimedia.org/wikipedia/commons/7/72/Fourier_transform_time_and_frequency_domains_%28small%29.gif

<https://www.youtube.com/watch?v=k8FXF1KjzY0>

Phasor Circulation and Sine/Cosine Wave

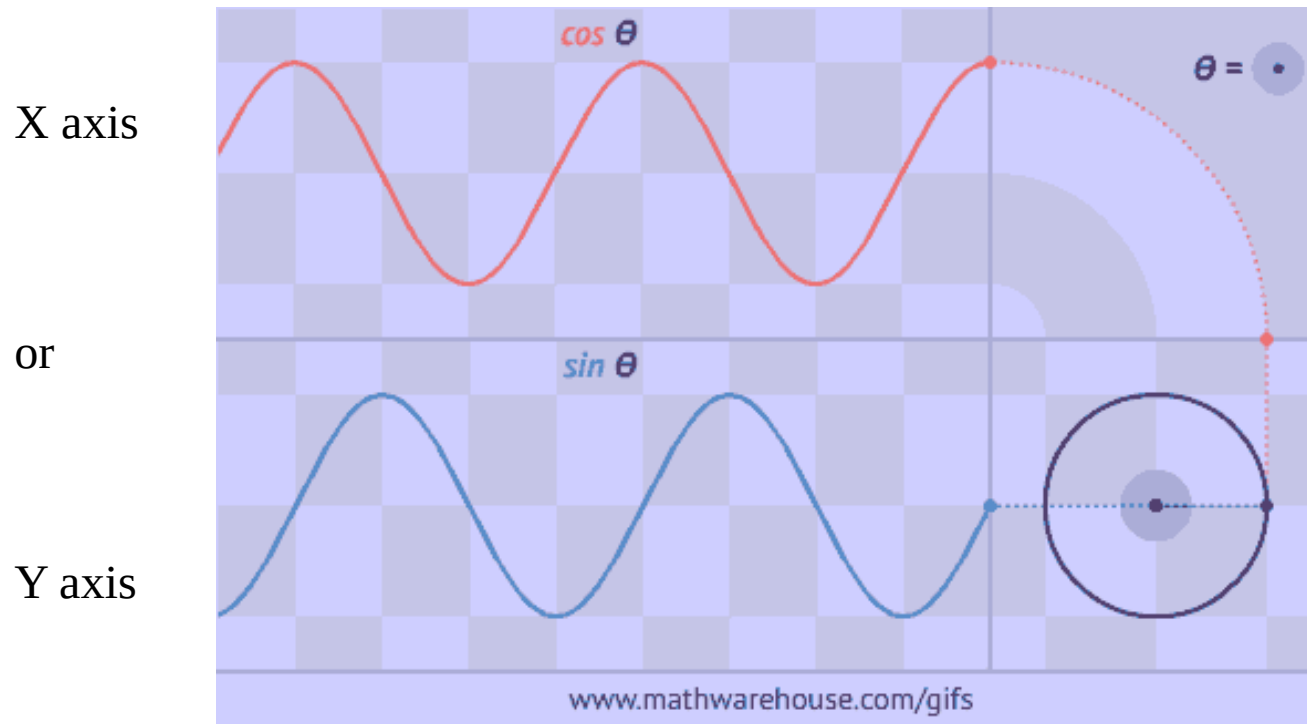- A phasor is a vector whose length is proportional to the maximum value of the variable.
- The phasor rotates counter-clockwise at the angular speed.




A Circulating vector
Phasor Diagram

Time or angle are the same if the angular speed of rotation is constant

<https://www.youtube.com/watch?v=Q55T6LeTvsA>

<http://demonstrations.wolfram.com/PlottingASineOrCosineWave/>

Description of Sine or Cosine Waves

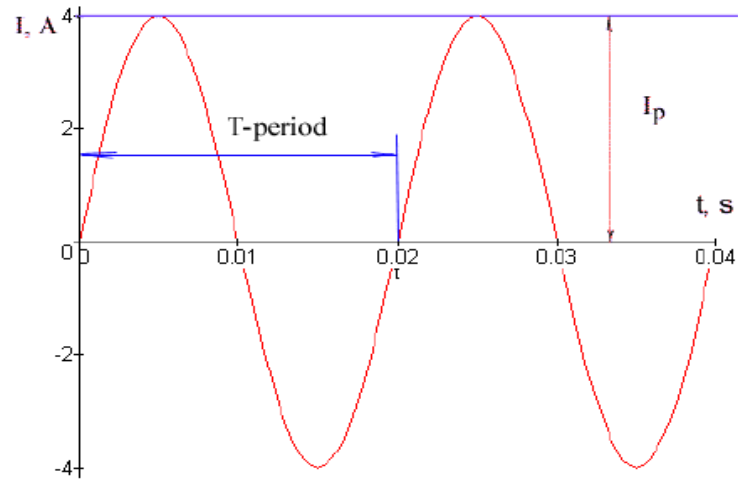

$$I(t) = I_{\max} \sin(\omega t) = I_{\max} \sin(2\pi f t),$$

$$I(t) = \sqrt{2} I_{\text{rms}} \sin(\omega t) = \sqrt{2} I_{\text{rms}} \sin(2\pi f t)$$

$$\sqrt{2} I_{\text{rms}} = I_{\max}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T_2 - T_1} \int_{T_1}^{T_2} (I_p \sin(\omega t))^2 dt}$$

Frequency/Period

Phase angle and displacement

Amplitude/Magnitude: RMS, Max,

- ▶ **AC (Alternating current):**
- ▶ **changing direction**
 - Transient
 - Steady-state or stationary
 - $\omega = 2\pi(60) = 377 \text{ s}^{-1}$ or rad/s
- ▶ **AC circuit components**
 - Resistor
 - Inductor (magnetic field)
 - Capacitor (electric field)
- ▶ **Phasor relations**
 - Phasor/phase
 - Leading, lag and in-phase

Review Basic Math Formulae

► Integrals and derivatives of trig. functions:

$$\frac{d \sin(\omega t)}{dt} = \omega \cos(\omega t)$$

$$\frac{d \cos(\omega t)}{dt} = -\omega \sin(\omega t)$$

$$\int \sin(\omega t) dt = -\frac{1}{\omega} \cos(\omega t)$$

$$\int \cos(\omega t) dt = \frac{1}{\omega} \sin(\omega t)$$

► Trigonometric Identities

$$\sin(\omega t + 90^\circ) = \cos(\omega t) \qquad \cos(\omega t + 90^\circ) = -\sin(\omega t)$$

$$\sin(\omega t - 90^\circ) = -\cos(\omega t) \qquad \cos(\omega t - 90^\circ) = \sin(\omega t)$$

$$\sin(x) \pm \sin(y) = 2 \sin\left(\frac{x \pm y}{2}\right) \cos\left(\frac{x \mp y}{2}\right)$$

$$\cos(x) + \cos(y) = 2 \cos\left(\frac{x + y}{2}\right) \cos\left(\frac{x - y}{2}\right)$$


$$\cos(x) - \cos(y) = -2 \sin\left(\frac{x + y}{2}\right) \sin\left(\frac{x - y}{2}\right)$$

Complete the following identities by yourself:

$\sin(x)\cos(y)$,
 $\sin(x)\sin(y)$ and
 $\cos(x)\sin(y)$



Frequency: 60 Hz vs 50 Hz

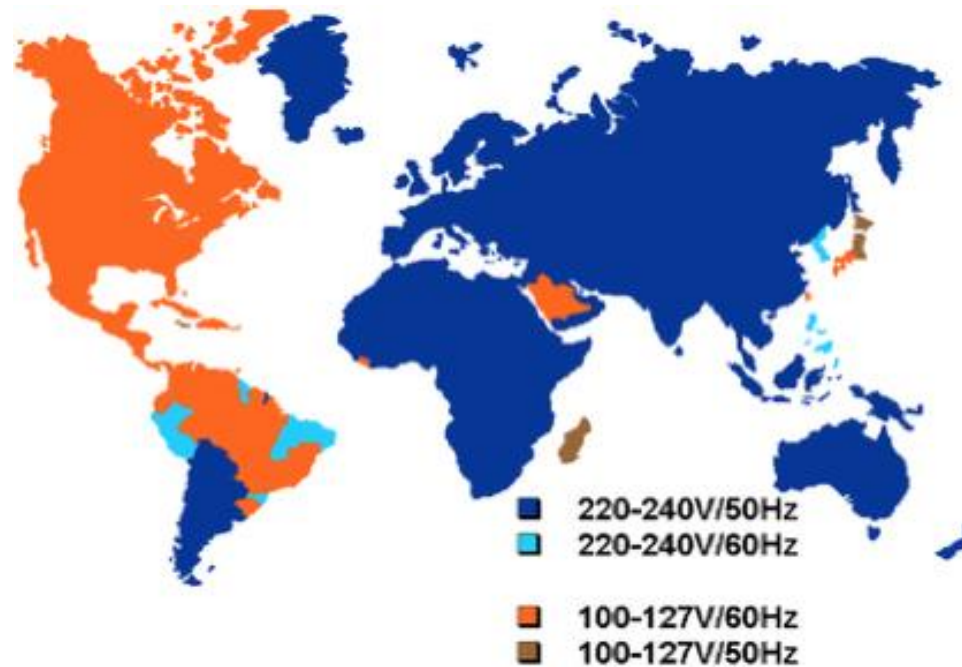- ▶ ω is an angular frequency.
 - $\omega = 2\pi f$ where f is the frequency in Hertz (Hz)
- ▶ In the US, the frequency is 60 Hz
 - $\omega = 2\pi(60) = 377 \text{ s}^{-1}$ or rad/s
- ▶ In Europe and some countries in Asia, 50 Hz or 314 s^{-1}




AC Circuit Structure

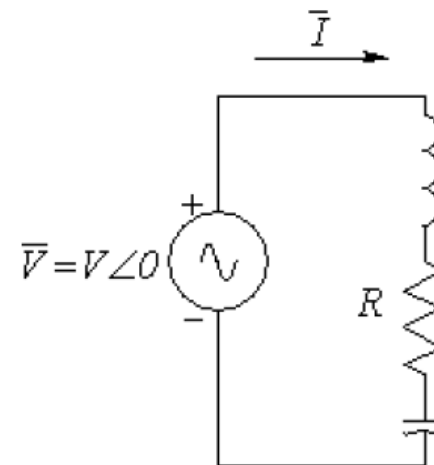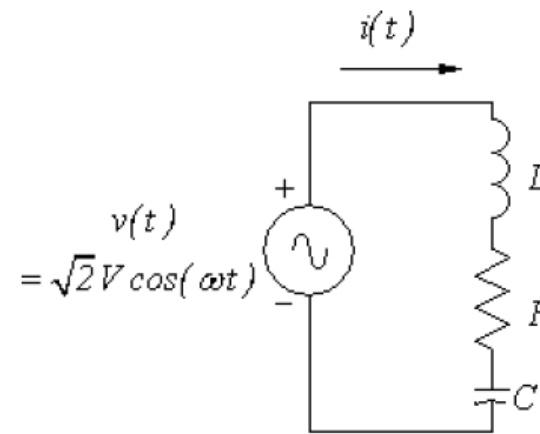- ▶ Calculate phasor domain impedance correspond to R, L, C.
- ▶ Find out the **frequency**, f
- ▶ Find **impedance angle**
- ▶ Plot **impedance triangle**




Phase: Phase Displacement of Voltage/Current

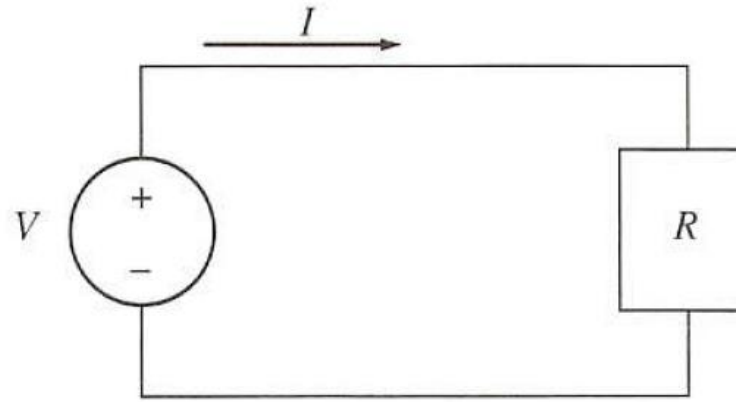- ▶ Voltage and Current
- ▶ In phase (pure resistor)
- ▶ Lagging current (positive impedance angle, inductive load)
- ▶ Leading current (negative impedance angle, capacitive load)




(a)

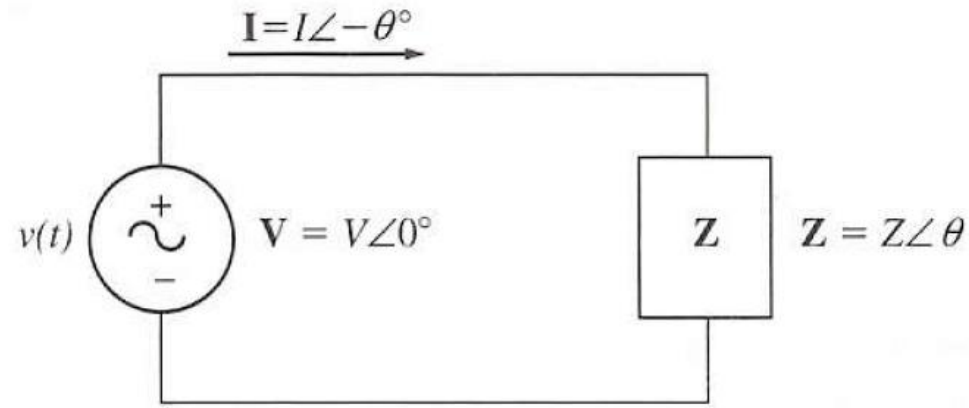


(b)

In Phase



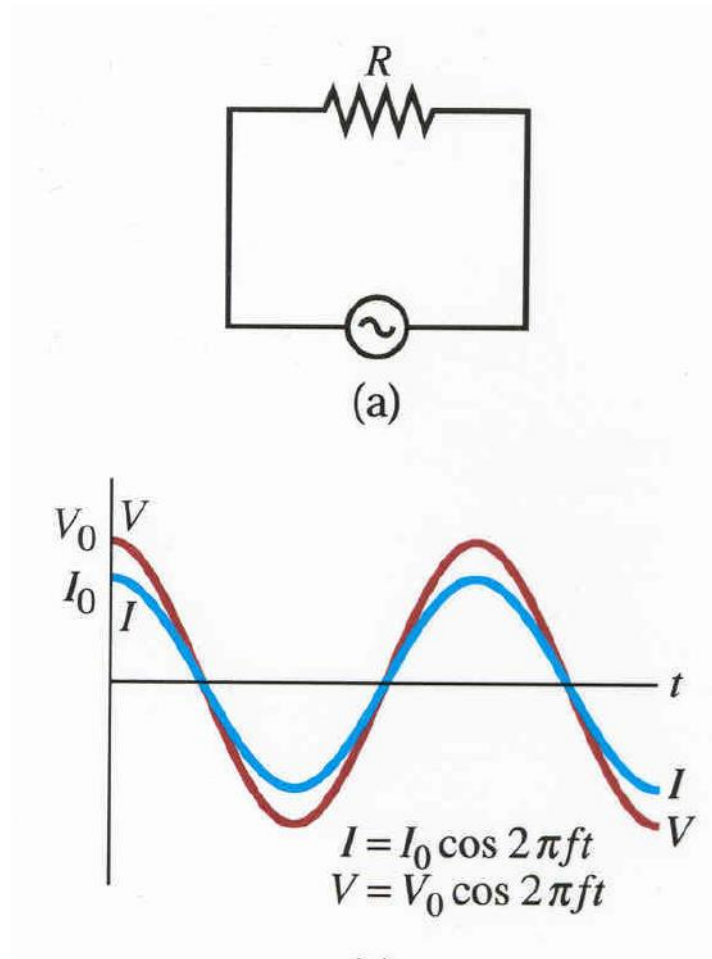


$$V_R = RI$$

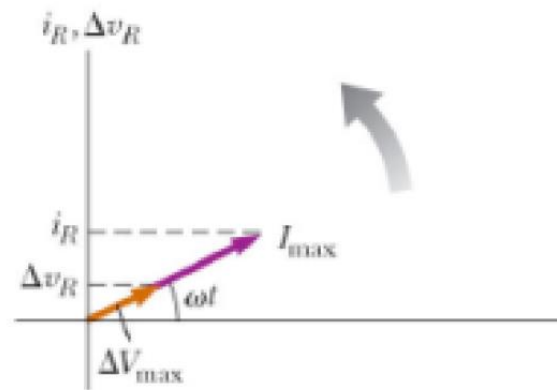


Lagging current


Inductor: current lags voltage

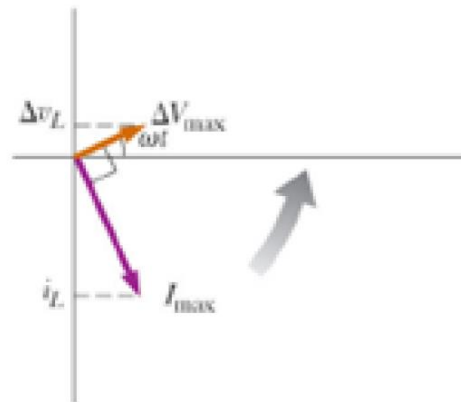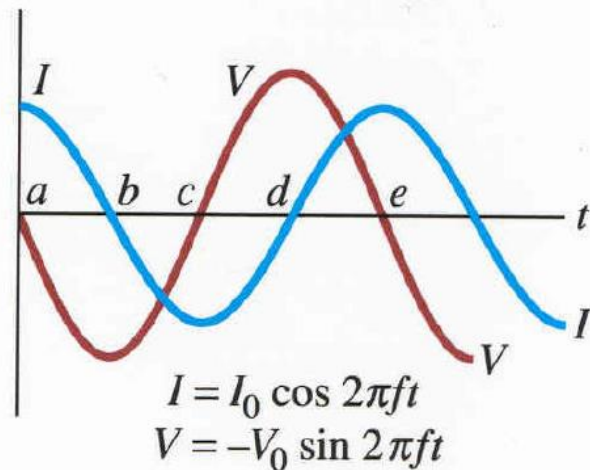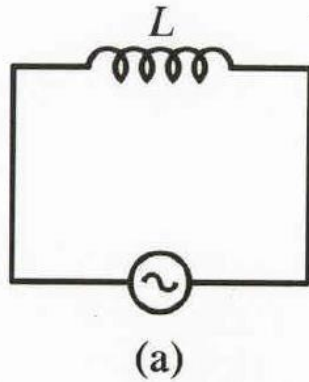

Leading Current

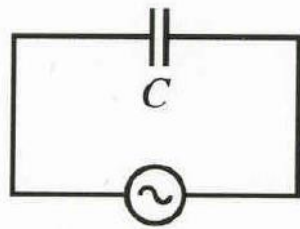


(a)

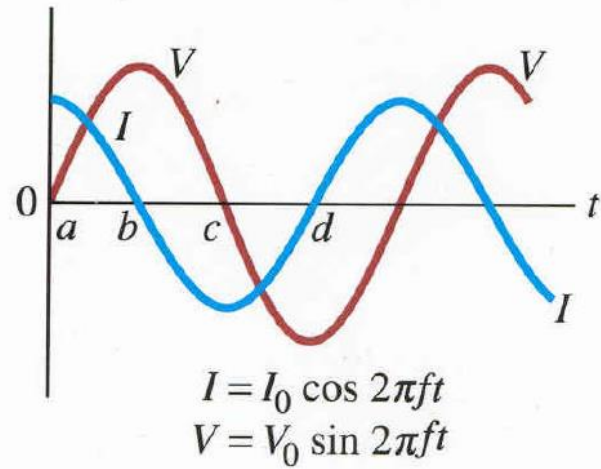

$$V_C = \frac{Q}{C} = \frac{1}{C} \int I dt$$


Capacitor: voltage lags current

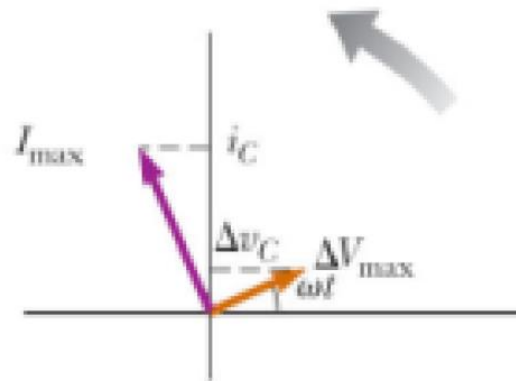

Power



Instantaneous Power

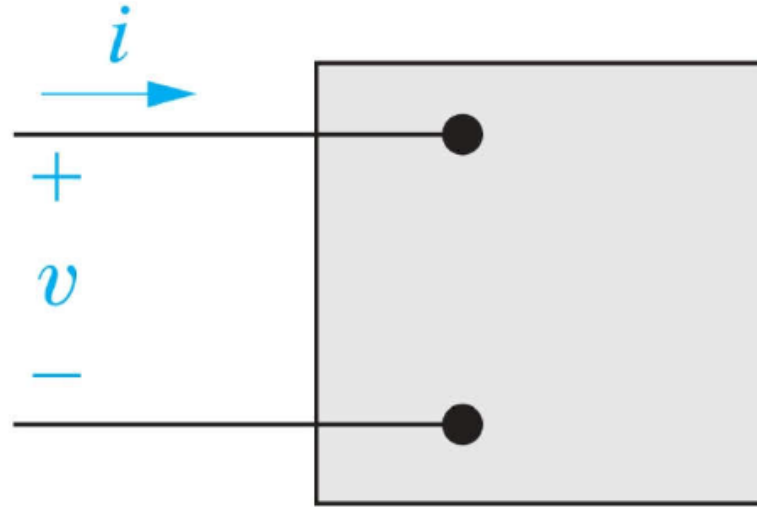


$$p = vi$$

$$v = V_m \cos(\omega t + \theta_v)$$

$$i = I_m \cos(\omega t + \theta_i)$$

Instantaneous Power

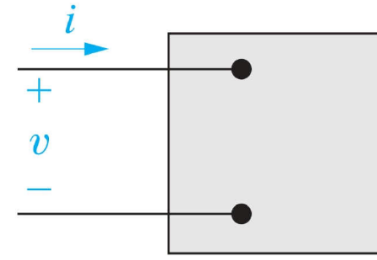

$$p = V_m \cos(\omega t + \theta_v - \theta_i) I_m \cos \omega t$$

$$p = vi$$

$$v = V_m \cos(\omega t + \theta_v)$$

$$i = I_m \cos(\omega t + \theta_i)$$

$$\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

p is at twice the frequency of
v and i

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$

Average and Reactive Power

$$p = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \longleftarrow \text{Average, or Real Power}$$

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \longleftarrow \text{Reactive Power}$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t$$

Real, Reactive, and Apparent Power in AC Circuits

- ▶ In a DC circuit, supplied power to the load is $P=VI$.
- ▶ In an AC circuit, the instantaneous power supplied to the
- ▶ load is given by...

$$\begin{aligned} p(t) &= v(t)i(t) = 2VI \cos \omega t \cos(\omega t - \theta) \\ &= \underbrace{VI \cos \theta (1 + \cos 2\omega t)}_{VI \cos \theta + "0"} + \underbrace{VI \sin \theta \sin 2\omega t}_{"0"} \end{aligned}$$

Real, Reactive, and Apparent Power in AC Circuits

- ▶ **Active or Real Power :**

$$P = V_{rms} I_{rms} \cos \theta = I_{rms}^2 Z \cos \theta = I_{rms}^2 R$$

- ▶ **Reactive Power :**

$$Q = V_{rms} I_{rms} \sin \theta = I_{rms}^2 Z \sin \theta = I_{rms}^2 X$$

- ▶ **Apparent Power :**

$$S = V_{rms} I_{rms}^{conj} = I_{rms}^2 Z = \sqrt{P^2 + Q^2} \text{ (scalar)}$$

- ▶ **Complex Power :**

$$S = V_{rms} I_{rms}^* = |V_{rms}| |I_{rms}| \cos \theta + j |V_{rms}| |I_{rms}| \sin \theta = P + jQ$$

where θ is impedance angle from...

$$Z = Z \angle \theta = Z \cos \theta + jZ \sin \theta = R + jX$$

Complex Power and Power Factor


$$S = |S|(\cos \theta + j \sin \theta) = P + jQ$$

Complex power:
VA, kVA, MVA

Active power:
W, kW, MW


Reactive power:
Var, kVar, MVar

$$|S| = \sqrt{P^2 + Q^2}$$

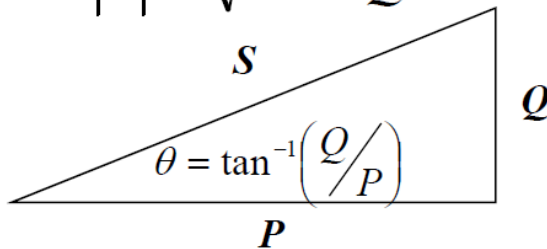

$$P = |S| \cos \theta$$

$$Q = |S| \sin \theta$$

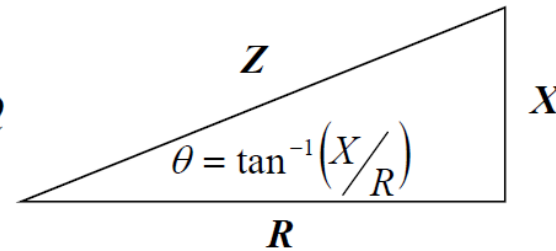

$$\text{Power factor} = \cos \theta = \frac{P}{|S|}$$

Lagging current:

$Q > 0, \theta > 0$, inductive

Leading current:

$Q < 0, \theta < 0$, capacitive

$P, Q^* > 0$:
consuming/absorbed

$P, Q^* < 0$:
producing/supplied


Power for Purely Resistive Circuits

- For a purely resistive circuit, the voltage and current are in phase.

$$\theta_v = \theta_i$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m I_m}{2}$$
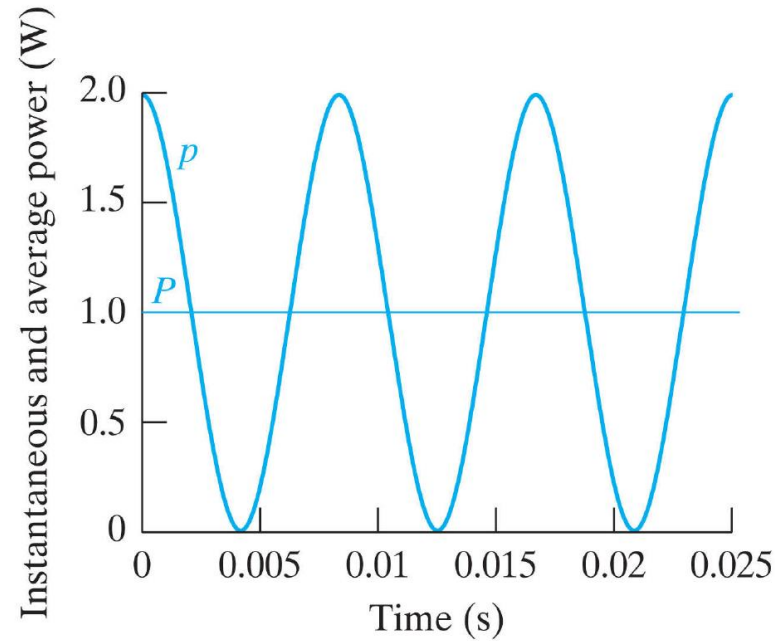
$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = 0$$



$$p = P + P \cos 2\omega t - Q \sin 2\omega t \rightarrow P + P \cos 2\omega t$$

Power for Purely Inductive Circuits

- ▶ Voltage and Current are out of phase by 90° .
- ▶ The current lags the voltage by 90° .


$$\theta_i = \theta_v - 90^\circ$$

$$\theta_v - \theta_i = +90^\circ$$

$$P = \frac{V_m I_m}{2} \cos(90^\circ) = 0$$

$$Q = \frac{V_m I_m}{2} \sin(90^\circ) = \frac{V_m I_m}{2}$$
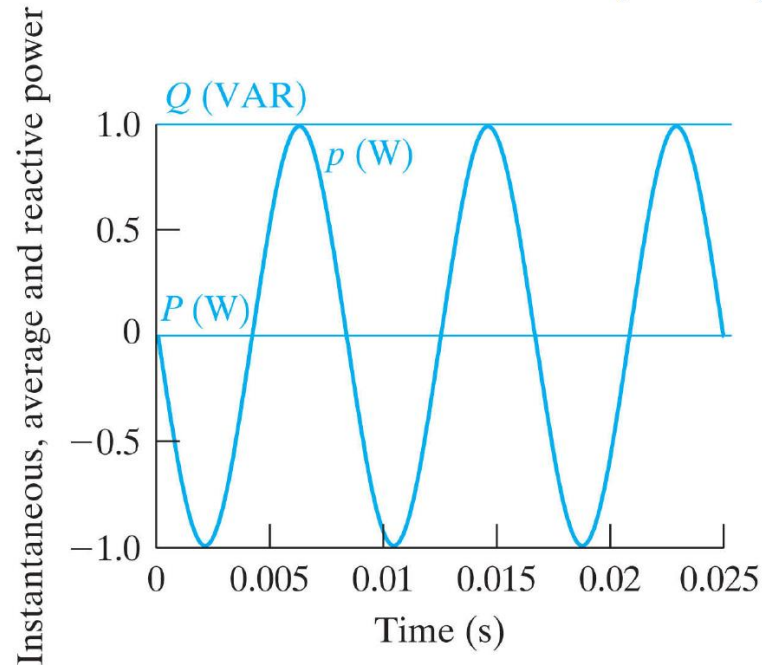
$$p = P + P \cos 2\omega t - Q \sin 2\omega t \rightarrow -Q \sin 2\omega t$$



Power for Purely Capacitive Circuits

- ▶ Voltage and Current out of phase by 90°
- ▶ The current leads the voltage by 90° .


$$\theta_i = \theta_v + 90^\circ$$

$$\theta_v - \theta_i = -90^\circ$$

$$P = \frac{V_m I_m}{2} \cos(-90^\circ) = 0$$

$$Q = \frac{V_m I_m}{2} \sin(-90^\circ) = -\frac{V_m I_m}{2}$$
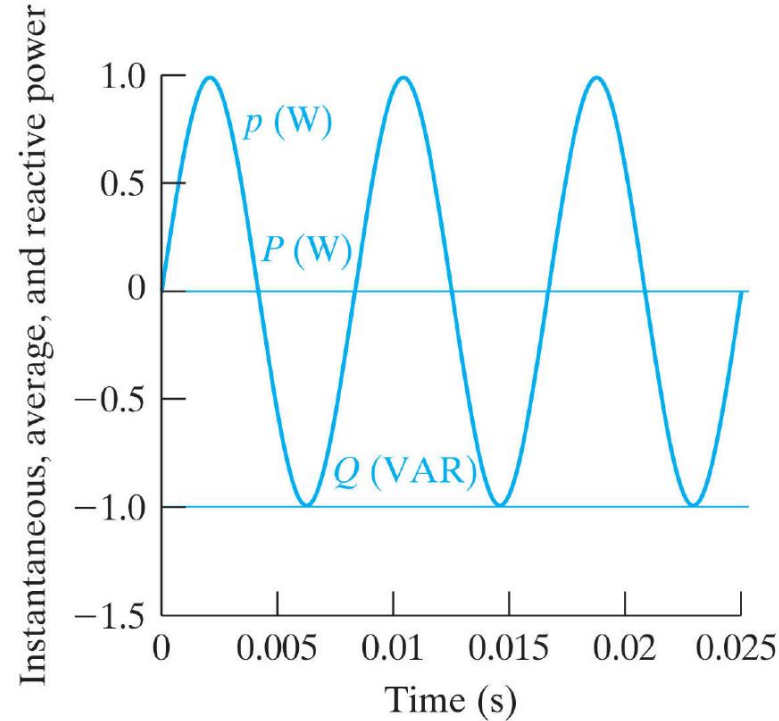
$$p = P + P \cos 2\omega t - Q \sin 2\omega t \rightarrow -Q \sin 2\omega t$$



Power Factor

▶ Power factor angle

$$\theta_v - \theta_i$$

▶ Power factor

$$pf = \cos(\theta_v - \theta_i)$$

▶ Reactive factor

$$rf = \sin(\theta_v - \theta_i)$$

▶ Lagging power factor

- Current Lags the Voltage
- Inductive Load

▶ Leading power factor

- Current Leads the Voltage
- Capacitive Load

Questions

